

### Half adder


- A half-adder is a combinational circuit with two binary inputs (augend and addend bits) and two binary outputs (sum and carry bits).
- It adds the two inputs (single bit words A and B) and produces the sum (S) and the carry (C) bits.
- The truth table of a half-adder are shown below:

Inputs		Outputs	
A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

- The Sum (S) is the X-OR of A and B (It represent the LSB of the sum). Therefore,  

$$S = AB' + BA' = A \oplus B$$
- The carry (C) is the AND of A and B (It is 0 unless both the inputs are 1). Therefore,  
 
$$C = AB$$
- A half-adder can, therefore, be realized by using one X-OR gate and one AND gate as shown in figure below.



### Full adder

- A full-adder is a combinational circuit that adds two bits and a carry and outputs a sum bit and a carry bit.
- When we want to add two binary numbers, each having two or more bits, the LSBs can be added by using a half-adder.
- The carry resulted from the addition of the LSBs is carried over to the next significant column and added to the two bits in that column.
- The full-adder adds the bits A and B and the carry from the previous column called the carry-in  $C_{in}$  and outputs the sum bit S and the carry bit called the carry-out  $C_{out}$ .
- The variable S gives the value of the least significant bit of the sum.
- The variable  $C_{out}$  gives the output carry.
- The truth table of a full-adder are shown in figure below.


Inputs			Outputs	
A	B	C <sub>in</sub>	S	C <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- The eight rows under the input variables designate all possible combinations of 1s and 0s that these variables may have.
- When all the bits are 0s, the output is 0.
- The S output is equal to 1 when only 1 input is equal to 1 or when all the inputs are equal to 1.
- The C<sub>out</sub> has a carry of 1 if two or three inputs are equal to 1.
- From the truth table, a circuit that will produce the correct sum and carry bits in response to every possible combination of A, B, and C<sub>in</sub> is described by

$$\begin{aligned}
 S &= A'B'C_{in} + A'BC_{in}' + AB'C_{in}' + ABC_{in} \\
 &= (A'B' + A'B)C_{in}' + (AB + A'B')C_{in} \\
 &= (A \oplus B)C_{in}' + (A \oplus B)'C_{in} \\
 &= A \oplus B \oplus C_{in}
 \end{aligned}$$

$$\begin{aligned}
 C_{out} &= A'BC_{in} + AB'C_{in} + ABC_{in}' + ABC_{in} \\
 &= AB + (A \oplus B)C_{in}
 \end{aligned}$$

 - The sum term of the full-adder is the X-OR of A, B and C<sub>in</sub>, i.e., the sum bit is the modulo sum of the data bits in that column and the carry from the previous column.
- The logic diagram of the full-adder using two X-OR gates and two AND gates (i.e., two half-adders) and one OR gate is shown in figure below.




### Half-Subtractor

- A half-subtractor is a combinational circuit that subtracts one bit from the other and produces the difference.
- It also has an output to specify if a 1 has been borrowed.
- It is used to subtract the LSB of the subtrahend from the LSB of the minuend when one binary number is subtracted from the other.
- A half-subtractor is a combinational circuit with two inputs A and B and two outputs  $d$  and  $b$ .
- $d$  indicates the difference and  $b$  is the output signal generated that informs the next stage that a 1 has been borrowed.
- We know that, when a bit B is subtracted from another bit A, a difference bit ( $d$ ) and a borrow bit ( $b$ ) result according to the rules given as follows.

Inputs		Outputs	
A	B	d	b
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

- A circuit that produces the correct difference and borrow bits in response to every possible combination of the two 1-bit numbers is, therefore, described by
- $$d = AB' + BA' = A \oplus B \text{ and } b = A'B$$
- That is, the difference bit is obtained by X-ORing the two inputs, and the borrow bit is obtained by ANDing the complement of the minuend with the subtrahend.
  - Figure below shows logic diagrams of a half-subtractor.

 

### Full Subtractor

- The half-subtractor can be used only for LSB subtraction.
- If there is a borrow during the subtraction of the LSBs, it affects the subtraction in the next higher column; the subtrahend bit is subtracted from the minuend bit, considering the borrow from that column used for the subtraction in the preceding column.
- Such a subtraction is performed by a full-subtractor.
- It subtracts one bit (B) from another bit (A), when already there is a borrow  $b_i$  from this column for the subtraction in the preceding column, and outputs the difference bit (d) and the borrow bit (b) required from the next column.
- So a full-subtractor is a combinational circuit with three inputs (A, B,  $b_i$ ) and two outputs d and b.
- The 1s and 0s for the output variables are determined from the subtraction of  $A - B - b_i$ .
- The truth table of a full-subtractor are shown in figure.


Inputs			Outputs	
A	B	$b_i$	d	b
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

- From the truth table, a circuit that will produce the correct difference and borrow bits in response to every possible combination of A, B, and  $b_i$  is described by

$$\begin{aligned}
 d &= A'B'b_i + A'Bb_i' + AB'b_i' + ABb_i \\
 &= (A'B' + A'B)b_i' + (AB + A'B')b_i \\
 &= (A \oplus B)b_i' + (A \oplus B)'b_i \\
 &= A \oplus B \oplus b_i
 \end{aligned}$$

$$\begin{aligned}
 b &= A'B'b_i + A'Bb_i' + A'Bb_i + ABb_i \\
 &= A'B(b_i + b_i') + (AB + A'B')b_i \\
 &= A'B + (A \oplus B)'b_i
 \end{aligned}$$

 - A full-subtractor can, therefore, be realized using X-OR gates as shown below.



### Design BCD to Excess-3 code converter circuit.

- BCD means 8421 BCD.
- The 4-bit input BCD code ( $B_4 B_3 B_2 B_1$ ) and the corresponding output XS-3 code ( $X_4 X_3 X_2 X_1$ ) numbers are shown in the conversion table in figure.

8421 code				XS-3 code			
$B_4$	$B_3$	$B_2$	$B_1$	$X_4$	$X_3$	$X_2$	$X_1$
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

- The input combinations 1010, 1011, 1100, 1101, 1110, and 1111 are invalid in BCD. So they are treated as don't cares.
- From the above truth table, function can be realized as follows:
 
$$X_4 = \sum m(5, 6, 7, 8, 9) + d(10, 11, 12, 13, 14, 15)$$

$$X_3 = \sum m(1, 2, 3, 4, 9) + d(10, 11, 12, 13, 14, 15)$$

$$X_2 = \sum m(0, 3, 4, 7, 8) + d(10, 11, 12, 13, 14, 15)$$

$$X_1 = \sum m(0, 2, 4, 6, 8) + d(10, 11, 12, 13, 14, 15)$$
- Drawing K-maps for the outputs  $X_4$ ,  $X_3$ ,  $X_2$ , and  $X_1$  in terms of the inputs  $B_4$ ,  $B_3$ ,  $B_2$ , and  $B_1$  and simplifying them, as shown.

		$B_2B_1$			
		00	01	11	10
$B_4B_3$	00	0	1	3	2
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10

$$X_4 = B_4 + B_3B_2 + B_3B_1$$

		$B_2B_1$			
		00	01	11	10
$B_4B_3$	00	0	1	3	2
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10

$$X_3 = B_3B_2'B_1' + B_3'B_1 + B_3'B_2$$

		$B_2B_1$			
		00	01	11	10
$B_4B_3$	00	0	1	3	2
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10

$$X_2 = B_2'B_1' + B_2B_1$$

		$B_2B_1$			
		00	01	11	10
$B_4B_3$	00	0	1	3	2
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10

$$X_1 = B_1'$$

- The minimal expressions are

$$X_4 = B_4 + B_3B_2 + B_3B_1$$

$$X_3 = B_3B_2'B_1' + B_3'B_1 + B_3'B_2$$

$$X_2 = B_2'B_1' + B_2B_1$$

$$X_1 = B_1'$$

### Design 4 bit binary to gray code converter

- The input to the 4-bit binary-to-Gray code converter circuit is a 4-bit binary and the output is a 4-bit Gray code.
- There are 16 possible combinations of 4-bit binary input and all of them are valid. Hence no don't cares.
- The 4-bit binary and the corresponding Gray code are shown in the conversion table below.

4-bit binary				4-bit Gray			
$B_4$	$B_3$	$B_2$	$B_1$	$G_4$	$G_3$	$G_2$	$G_1$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1

0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0

- From the conversion table, we observe that the expressions for the outputs G4, G3, G2, and G1 are as follows:

$$G_4 = \sum m(8, 9, 10, 11, 12, 13, 14, 15)$$

$$G_3 = \sum m(4, 5, 6, 7, 8, 9, 10, 11)$$

$$G_2 = \sum m(2, 3, 4, 5, 10, 11, 12, 13)$$

$$G_1 = \sum m(1, 2, 5, 6, 9, 10, 13, 14)$$

- The K-maps for G4, G3, G2, and G1 and their minimization are shown in figure below.

		$B_2B_1$			
		00	01	11	10
$B_4B_3$	00	0	1	3	2
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10

$$G_4 = B_4$$

		$B_2B_1$			
		00	01	11	10
$B_4B_3$	00	0	1	3	2
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10

$$G_3 = B_4 \oplus B_3$$

	$B_2B_1$			
	00	01	11	10
$B_4B_3$				
00	0	1	3	2
			1	1
01	4	5	7	6
	1	1		
11	12	13	15	14
	1	1		
10	8	9	11	10
			1	1

$$G_2 = B_3 \oplus B_2$$

	$B_2B_1$			
	00	01	11	10
$B_4B_3$				
00	0	1	3	2
		1		1
01	4	5	7	6
		1		1
11	12	13	15	14
		1		1
10	8	9	11	10
		1		1

$$G_1 = B_2 \oplus B_1$$

- The minimal expressions for the outputs obtained from the K-map are:


$$G_4 = B_4$$

$$G_3 = B_4'B_3 + B_4B_3' = B_4 \oplus B_3$$

$$G_2 = B_3'B_2 + B_3B_2' = B_3 \oplus B_2$$

$$G_1 = B_2'B_1 + B_2B_1' = B_2 \oplus B_1$$

 - Logic diagram for the above is as follows.




### Design a circuit for 2-bit magnitude comparator.

- The logic for a 2-bit magnitude comparator: Let the two 2-bit numbers be  $A = A_1A_0$  and  $B = B_1B_0$ .
  - If  $A_1 = 1$  and  $B_1 = 0$ , then  $A > B$  or
  - If  $A_1$  and  $B_1$  coincide and  $A_0 = 1$  and  $B_0 = 0$ , then  $A > B$ . So the logic expression for  $A > B$  is
 
$$A > B : G = A_1B_1' + (A_1 \odot B_1) A_0B_0'$$
  - If  $A_1 = 0$  and  $B_1 = 1$ , then  $A < B$  or
  - If  $A_1$  and  $B_1$  coincide and  $A_0 = 0$  and  $B_0 = 1$ , then  $A < B$ . So the expression for  $A < B$  is
 
$$A < B : L = A_1'B_1 + (A_1 \odot B_1) A_0'B_0$$

If  $A_1$  and  $B_1$  coincide and if  $A_0$  and  $B_0$  coincide then  $A = B$ . So the expression for  $A = B$  is

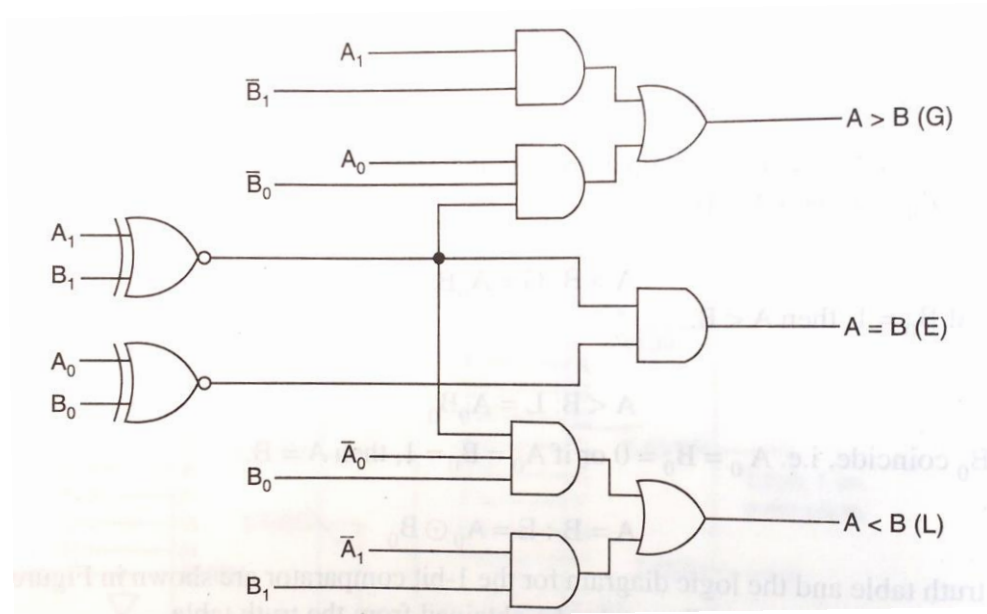
$$A = B : E = (A_1 \odot B_1)(A_0 \odot B_0)$$
- The logic diagram for a 2-bit comparator is as shown below:






 **Draw & explain in brief pin diagram of 7485 four-bit magnitude comparator.**

- Figure below shows the pin diagram of IC 7485, a 4-bit comparator.



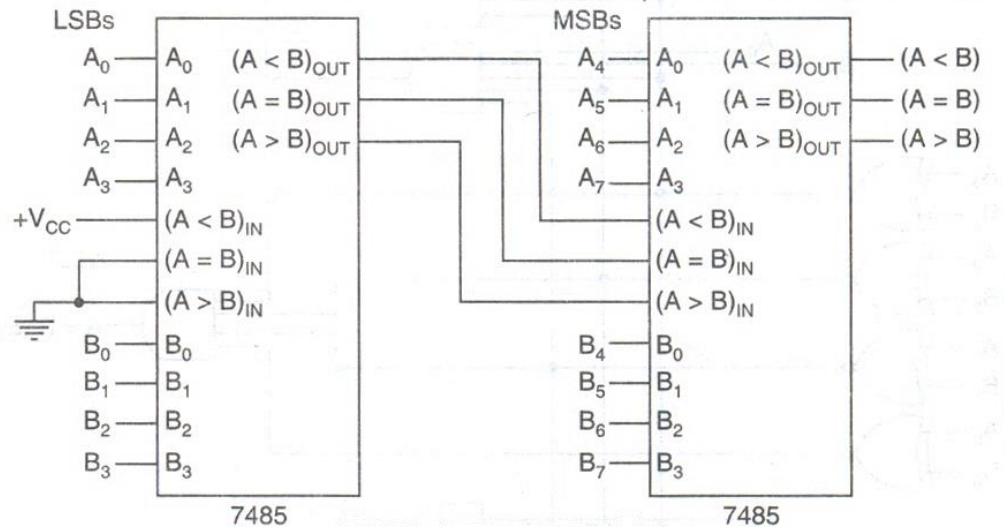- Pins labelled  $(A < B)_{IN}$ ,  $(A = B)_{IN}$ , and  $(A > B)_{IN}$  are used for cascading.
- Figure shows how two 4-bit comparator are cascaded to perform 8-bit comparisons.




- The  $(A < B)_{OUT}$ ,  $(A = B)_{OUT}$  and  $(A > B)_{OUT}$  outputs from the lower order comparator used for the least significant 4 bits, are connected to the  $(A < B)_{IN}$ ,  $(A = B)_{IN}$ , and  $(A > B)_{IN}$  inputs of the higher-order comparator.
- Note that,  $(A < B)_{IN}$  input of the lower order comparator is connected to  $V_{CC}$ , and  $(A = B)_{IN}$  and  $(A > B)_{IN}$  inputs of the lower order comparator are connected to ground.
 
### What is multiplexer? With logic circuit and function table explain the working of 4 to 1 line multiplexer.

- A multiplexer (MUX) is a device that allows digital information from several sources to be routed onto a single line for transmission over that line to a common destination.
- Consider an integer 'm', which is constrained by the following relation:  

$$m = 2^n$$
 where m and n are both integers.
- A **m-to-1** Multiplexer has
  - m Inputs:  $I_0, I_1, I_2, \dots, I_{(m-1)}$
  - One Output: Y
  - n Control inputs:  $S_0, S_1, S_2, \dots, S_{(n-1)}$
  - One (or more) Enable input(s)
 such that Y may be equal to one of the inputs, depending upon the control inputs.
- The block diagram of 4 x 1 multiplexer is as follows.




- The function table for the 4 x 1 multiplexer can be stated as below.

Select Inputs		Output
$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

- The following logic function describes the above function table.

$$Y = S_1' S_0' I_0 + S_1' S_0 I_1 + S_1 S_0' I_2 + S_1 S_0 I_3$$

 - The following figure describes the logic circuit for 4 x 1 multiplexer.



- Applications of Multiplexer is as follows:
  1. Logic function generation
  2. Data selection
  3. Data routing
  4. Operation sequencing
  5. Parallel-to-serial conversion
  6. Waveform generation


**Implement following Boolean function using 8 : 1 multiplexer.**

$$F(A,B,C,D) = \Sigma(2,3,5,7,8,9,12,13,14,15)$$

- The truth table for the above function is as follows:

S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	D	F	
A	B	C			
0	0	0	0	0	F = 0
0	0	0	1	0	
0	0	1	0	1	F = 1
0	0	1	1	1	
0	1	0	0	0	F = D
0	1	0	1	1	
0	1	1	0	0	F = D
0	1	1	1	1	
1	0	0	0	1	F = 1
1	0	0	1	1	
1	0	1	0	0	F = 0
1	0	1	1	0	
1	1	0	0	1	F = 1
1	1	0	1	1	
1	1	1	0	1	F = 1
1	1	1	1	1	

 - Based on the above truth table, the logic function can be implemented using 8 x 1 Multiplexer as follows:




### Exercise

Implement following Boolean function using 8 : 1 multiplexer.

- 1)  $F(A, B, C) = \sum m(1, 3, 5, 6)$
- 2)  $F(A, B, C) = \sum m(1, 2, 4, 7)$
- 3)  $F(A, B, C, D) = \sum m(0, 1, 3, 5, 7, 11, 13, 14, 15)$
- 4)  $F(A, B, C, D) = \sum m(0, 1, 2, 3, 5, 8, 9, 11, 14)$
- 5)  $F(A, B, C, D) = \sum m(0, 1, 3, 4, 8, 9, 15)$
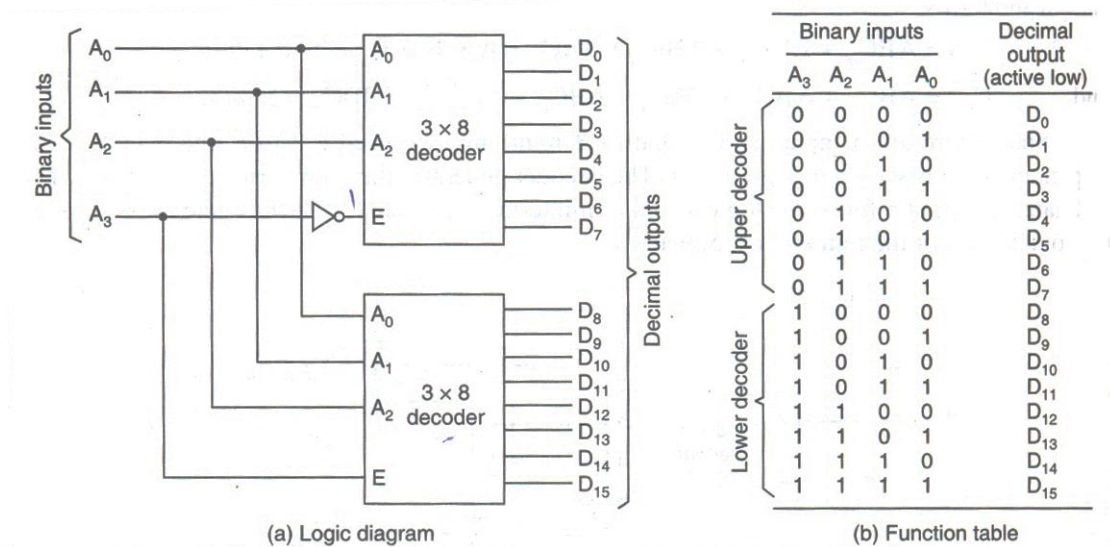
### Design 4 x 16 decoder using two 3 x 8 decoder.

- Decoders with enable inputs can be connected together to form a larger decoder circuit.
- Figure shows the arrangement for using two 3-to-8 decoders, to obtain a 4-to-16 decoder.
- The most significant input bit  $A_3$  is connected through an inverter to E on the upper decoder (for  $D_0$  through  $D_7$ ) and directly to E on the lower decoder (for  $D_8$  through  $D_{15}$ ).
- Thus, when  $A_3$  is LOW, the upper decoder is enabled and the lower decoder is disabled.
- The bottom decoder outputs all 0s, and top 8 outputs generate minterms.
- When  $A_3$  is HIGH, the lower decoder is enabled and the upper decoder is disabled. The bottom decoder outputs generate minterms 1000 to 1111 while the outputs of the top decoder are all 0s.



**Explain full adder and design a full adder circuit using 3 to 8 decoder and two OR gates.**


- A full-adder is a combinational circuit that adds two bits and a carry and outputs a sum bit and a carry bit.
- When we want to add two binary numbers, each having two or more bits, the LSBs can be added by using a half-adder.
- The carry resulted from the addition of the LSBs is carried over to the next significant column and added to the two bits in that column.
- The full-adder adds the bits A and B and the carry from the previous column called the carry-in  $C_{in}$  and outputs the sum bit S and the carry bit called the carry-out  $C_{out}$ .
- The variable S gives the value of the least significant bit of the sum.
- The variable  $C_{out}$  gives the output carry.
- The truth table of a full-adder are shown in figure below.

Inputs			Outputs	
A	B	$C_{in}$	S	$C_{out}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- The eight rows under the input variables designate all possible combinations of 1s and 0s that these variables may have.
- When all the bits are 0s, the output is 0.
- The S output is equal to 1 when only 1 input is equal to 1 or when all the inputs are equal to 1.
- The  $C_{out}$  has a carry of 1 if two or three inputs are equal to 1.
- From the truth table, a circuit that will produce the correct sum and carry bits in response to every possible combination of A, B, and  $C_{in}$  is described by
- The function S and  $C_{out}$  can be represented in form of minterms as,  

$$S = \sum m(1, 2, 4, 7)$$
 
$$C_{out} = \sum m(3, 5, 6, 7)$$
- The full adder can be implemented using decoder is as follows.



### Implement Full Subtractor Circuit with the help of Decoder and logic gates.

- The half-subtractor can be used only for LSB subtraction.
- If there is a borrow during the subtraction of the LSBs, it affects the subtraction in the next higher column; the subtrahend bit is subtracted from the minuend bit, considering the borrow from that column used for the subtraction in the preceding column.
- Such a subtraction is performed by a full-subtractor.
- It subtracts one bit (B) from another bit (A), when already there is a borrow  $b_i$  from this column for the subtraction in the preceding column, and outputs the difference bit (d) and the borrow bit (b) required from the next column.
- So a full-subtractor is a combinational circuit with three inputs (A, B,  $b_i$ ) and two outputs d and b.
- The 1s and 0s for the output variables are determined from the subtraction of  $A - B - b_i$ .
- The truth table of a full-subtractor are shown in figure.

Inputs			Outputs	
A	B	$b_i$	d	b
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

- From the truth table, a circuit that will produce the correct difference and borrow bits in response to every possible combination of A, B, and  $b_i$  is described by
- The function d and b can be represented in form of minterms as,  

$$d = \sum m(1, 2, 4, 7)$$

$$b = \sum m(1, 2, 3, 7)$$
- The full subtractor can be implemented using decoder is as follows.

