

Design of synchronous counters.

- **Step 1. Number of flip-flops:**
Based on the description of the problem, determine the required number n of the FFs - the smallest value of n is such that the number of states $N \leq 2^n$ and the desired counting sequence.
- **Step 2. State diagram:**
Draw the state diagram showing all the possible states.
- **Step 3. Choice of flip-flops and excitation table:**
Select the type of flip-flops to be used and write the excitation table.
An excitation table is a table that lists the present state (PS), the next state (NS) and the required excitations.
- **Step 4. Minimal expressions for excitations:**
Obtain the minimal expressions for the excitations of the FFs using K-maps for the excitations of the flip-flops in terms of the present states and inputs.
- **Step 5. Logic Diagram:**
Draw the logic diagram based on the minimal expressions.
- **Excitation Tables**

PS	NS	Required inputs	
Q_n	Q_{n+1}	S	R
0	0	0	x
0	1	1	0
1	0	0	1
1	1	x	0

S-R FF

PS	NS	Required inputs	
Q_n	Q_{n+1}	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

J-K FF

PS	NS	Required inputs
Q_n	Q_{n+1}	D
0	0	0
0	1	1
1	0	0
1	1	1

D FF

PS	NS	Required inputs
Q_n	Q_{n+1}	T
0	0	0
0	1	1
1	0	1
1	1	0


T FF

Design a counter to generate the repetitive sequence 0,1,2,4,3,6.

Step 1. Number of flip-flops:

A counter with repetitive sequence 0, 1, 2, 4, 3, 6 requires 3 flip-flops. The counting sequence is 000, 001, 010, 100, 011, 110, 000 ...

Step 2. Draw the state diagram:

 


Step 3. Select the type of flip-flops and draw the excitation table:

T flip-flops are selected and the excitation table of a given sequence counter using T flip-flops is shown below.

PS			NS			Required excitations		
Q_3	Q_2	Q_1	Q_3	Q_2	Q_1	T_3	T_2	T_1
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	1	0	0	1	1	0
1	0	0	0	1	1	1	1	1
0	1	1	1	1	0	1	0	1
1	1	0	0	0	0	1	1	0

Step 4. Obtain the minimal expressions

 K – Maps for excitations T_3 , T_2 , and T_1 and their minimized form are as follows:




Q_2Q_1		00	01	11	10
Q_3	0		1		1
	1	1	x	x	1

$$T_2 = Q_3 + Q_1Q_2' + Q_1'Q_2$$

Q_2Q_1		00	01	11	10
Q_3	0	1	1	1	
	1	1	x	x	

$$T_1 = Q_2' + Q_1$$

Step 5. Draw the logic diagram

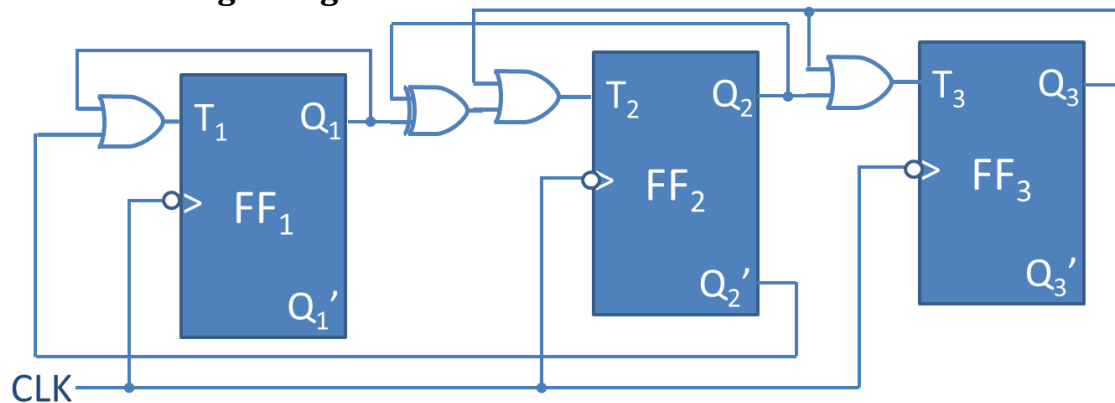


Design 3-bit synchronous up counter using T flip flop.

Step 1. Number of flip-flops:

A 3 bit up counter requires 3 flip-flops. The counting sequence is 000, 001, 010, 011, 100, 101, 110, 111, 000 ...

Step 2. Draw the state diagram:

 

Step 3. Select the type of flip-flops and draw the excitation table:

T flip-flops are selected and the excitation table of a given sequence counter using T flip-flops is shown below.

PS			NS			Required excitations		
Q_3	Q_2	Q_1	Q_3	Q_2	Q_1	T_3	T_2	T_1
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

Step 4. Obtain the minimal expressions

From excitation table, $T_1 = 1$.

K – Maps for excitations T_3 and T_2 and their minimized form are as follows:


		Q_2Q_1			
		00	01	11	10
Q_3	0		1	1	
	1		1	1	

$T_2 = Q_1$

Q_2Q_1	00	01	11	10
Q_3				
0			1	
1			1	

$T_3 = Q_1Q_2$

Step 5. Draw the logic diagram

 


Design a synchronous BCD counter with JK flip-flops.

Step 1. Number of flip-flops:

A BCD counter requires 4 flip-flops. The counting sequence is 0000, 0001, 0010, 0011, 0100, 0101, 0110, 0111, 1000, 1001, 0000 ...

Step 2. Draw the state diagram:

 

Step 3. Select the type of flip-flops and draw the excitation table:

J-K flip-flops are selected and the excitation table of a given sequence counter using J-K flip-flops is shown below.

PS				NS				Required excitations							
Q ₄	Q ₃	Q ₂	Q ₁	Q ₄	Q ₃	Q ₂	Q ₁	J ₄	K ₄	J ₃	K ₃	J ₂	K ₂	J ₁	K ₁
0	0	0	0	0	0	0	1	0	x	0	x	0	x	1	x
0	0	0	1	0	0	1	0	0	x	0	x	1	x	x	1
0	0	1	0	0	0	1	1	0	x	0	x	x	0	1	x
0	0	1	1	0	1	0	0	0	x	1	x	x	1	x	1
0	1	0	0	0	1	0	1	0	x	x	0	0	x	1	x
0	1	0	1	0	1	1	0	0	x	x	0	1	x	x	1
0	1	1	0	0	1	1	1	0	x	x	0	x	0	1	x
0	1	1	1	1	0	0	0	1	x	x	1	x	1	x	1
1	0	0	0	1	0	0	1	x	0	0	x	0	x	1	x
1	0	0	1	0	0	0	0	x	1	0	x	0	x	x	1

Step 4. Obtain the minimal expressions

From excitation table, it is clear that $J_1 = K_1 = 1$

K – Maps for excitations $J_4, K_4, J_3, K_3, J_2, K_2, J_1$ and K_1 and their minimized form are as follows:

Q_2Q_1	00	01	11	10
Q_4Q_3				
00				
01			1	
11	x	x	x	x
10	x	x	x	x

$$J_4 = Q_3Q_2Q_1$$

Q_2Q_1	00	01	11	10
Q_4Q_3				
00	x	x	x	x
01	x	x	x	x
11	x	x	x	x
10		1	x	x

$$K_4 = Q_1$$

Q_2Q_1	00	01	11	10
Q_4Q_3				
00			1	
01	x	x	x	x
11	x	x	x	x
10			x	x

$$J_3 = Q_1Q_2$$

Q_2Q_1	00	01	11	10
Q_4Q_3				
00	x	x	x	x
01			1	
11	x	x	x	x
10	x	x	x	x

$$K_3 = Q_1Q_2$$


Q_2Q_1	00	01	11	10
Q_4Q_3				
00		1	x	x
01		1	x	x
11	x	x	x	x
10			x	x

$$J_2 = Q_1Q_4'$$

Q_2Q_1	00	01	11	10
Q_4Q_3				
00	x	x	1	
01	x	x	1	
11	x	x	x	x
10	x	x	x	x

$$K_2 = Q_1$$

Step 5. Draw the logic diagram

 


Design a 3-bit synchronous up counter using K-maps and positive edge-triggered JK FFs.

Step 1. Number of flip-flops:

A 3 bit up counter requires 3 flip-flops. The counting sequence is 000, 001, 010, 011, 100, 101, 110, 111, 000 ...

Step 2. Draw the state diagram:

 

Step 3. Select the type of flip-flops and draw the excitation table:

J-K flip-flops are selected and the excitation table of a given sequence counter using J-K flip-flops is shown below.

PS			NS			Required excitations					
Q ₃	Q ₂	Q ₁	Q ₃	Q ₂	Q ₁	J ₃	K ₃	J ₂	K ₂	J ₁	K ₁
0	0	0	0	0	1	0	x	0	x	1	x
0	0	1	0	1	0	0	x	1	x	x	1
0	1	0	0	1	1	0	x	x	0	1	x
0	1	1	1	0	0	1	x	x	1	x	1
1	0	0	1	0	1	x	0	0	x	1	x
1	0	1	1	1	0	x	0	1	x	x	1
1	1	0	1	1	1	x	0	x	0	1	x
1	1	1	0	0	0	x	1	x	1	x	1

Step 4. Obtain the minimal expressions

From excitation table, $J_1 = K_1 = 1$.

K – Maps for excitations J_3 , K_3 , J_2 and K_2 and their minimized form are as follows:

Q_2Q_1	00	01	11	10
Q_3 0			1	
Q_3 1	x	x	x	x

$$J_3 = Q_2Q_1$$

Q_2Q_1	00	01	11	10
Q_3 0	x	x	x	x
Q_3 1			1	

$$K_3 = Q_2Q_1$$


Q_2Q_1	00	01	11	10
Q_3 0		1	x	x
Q_3 1		1	x	x

$$J_2 = Q_1$$

Q_2Q_1	00	01	11	10
Q_3 0	x	x	1	
Q_3 1	x	x	1	

$$K_2 = Q_1$$

Step 5. Draw the logic diagram

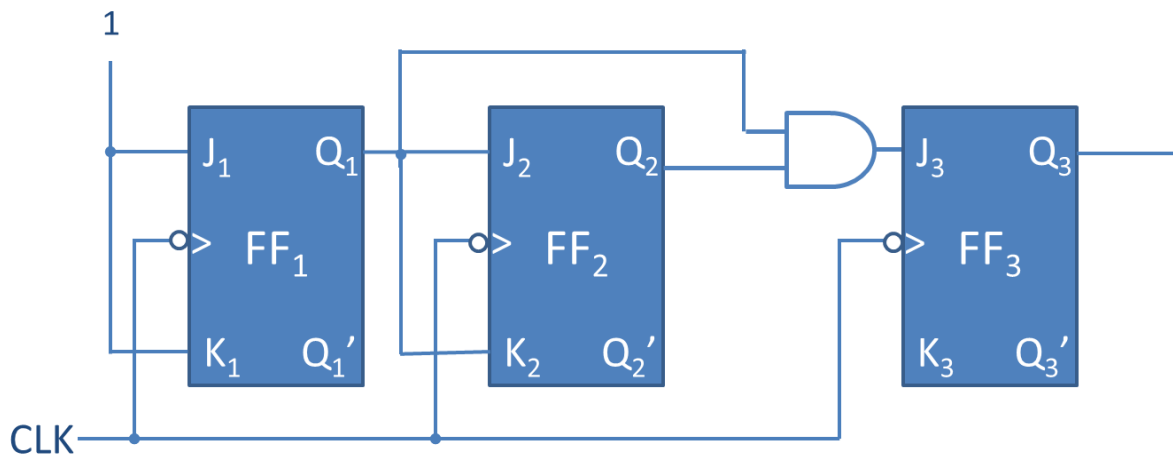


Design a mod-12 Synchronous up counter using D-flipflop.

Step 1. Number of flip-flops:

A mod-12 counter requires 4 flip-flops. The counting sequence is 0000, 0001, 0010, 0011, 0100, 0101, 0110, 0111, 1000, 1001, 1010, 1011, 0000 ...

Step 2. Draw the state diagram:

 

Step 3. Select the type of flip-flops and draw the excitation table:

D flip-flops are selected and the excitation table of a given sequence counter using D flip-flops is shown below.

PS				NS				Required excitations			
Q ₄	Q ₃	Q ₂	Q ₁	Q ₄	Q ₃	Q ₂	Q ₁	D ₄	D ₃	D ₂	D ₁
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	1	0	0	1	0	0	0	1	0
0	0	1	0	0	0	1	1	0	0	1	1
0	0	1	1	0	1	0	0	0	1	0	0
0	1	0	0	0	1	0	1	0	1	0	1
0	1	0	1	0	1	1	0	0	1	1	0
0	1	1	0	0	1	1	1	0	1	1	1
0	1	1	1	1	0	0	0	1	0	0	0
1	0	0	0	1	0	0	1	1	0	0	1
1	0	0	1	1	0	1	0	1	0	1	0
1	0	1	0	1	0	1	1	1	0	1	1
1	0	1	1	0	0	0	0	0	0	0	0

Step 4. Obtain the minimal expressions

K – Maps for excitations D₄, D₃, D₂, and D₁ and their minimized form are as follows:

Q_2Q_1	00	01	11	10
Q_4Q_3				
00				
01			1	
11	x	x	x	x
10	1	1		1

$$D_4 = Q_2'Q_4 + Q_1'Q_4 + Q_1Q_2Q_3$$

Q_2Q_1	00	01	11	10
Q_4Q_3				
00			1	
01	1	1		1
11	x	x	x	x
10				

$$D_3 = Q_2'Q_3 + Q_1'Q_3 + Q_1Q_2Q_3'Q_4'$$

Q_2Q_1	00	01	11	10
Q_4Q_3				
00		1		1
01		1		1
11	x	x	x	x
10		1		1

$$D_2 = Q_2'Q_1 + Q_2Q_1'$$

Q_2Q_1	00	01	11	10
Q_4Q_3				
00	1			1
01	1			1
11	x	x	x	x
10	1			1

$$D_1 = Q_1'$$

Step 5. Draw the logic diagram

